

DESIGN AND SIMULATION OF SERIES RESONANT CONVERTER FOR EV CHARGING

Sonu Kumar (231040108)


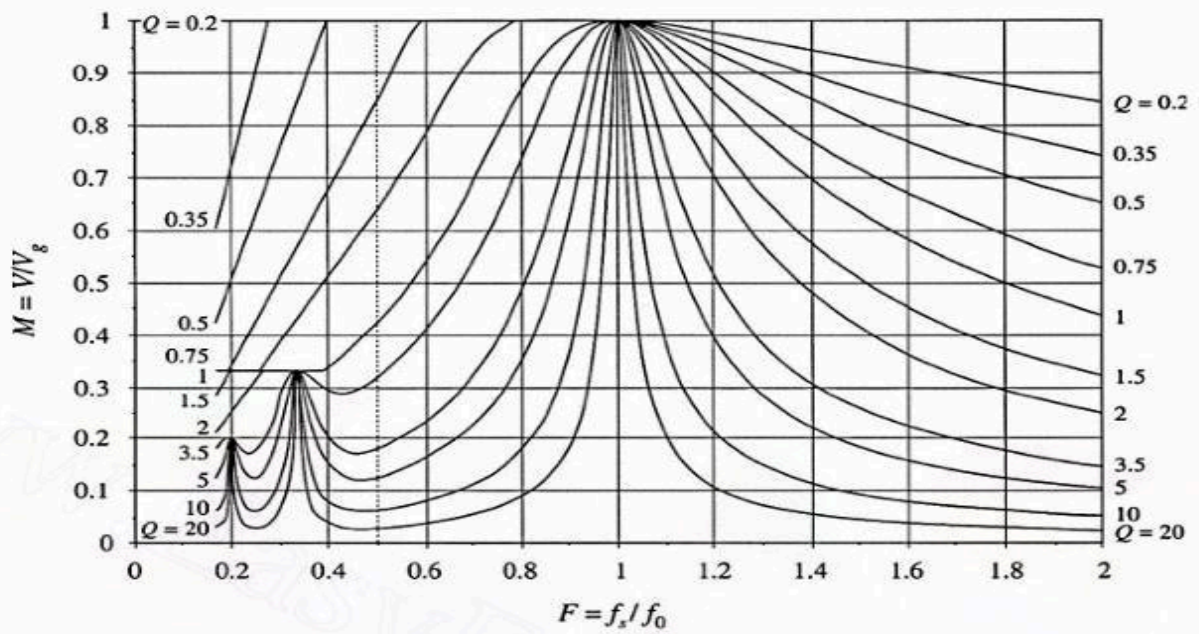


Figure 1 : M vs F for different Q values

Theoretical Calculations

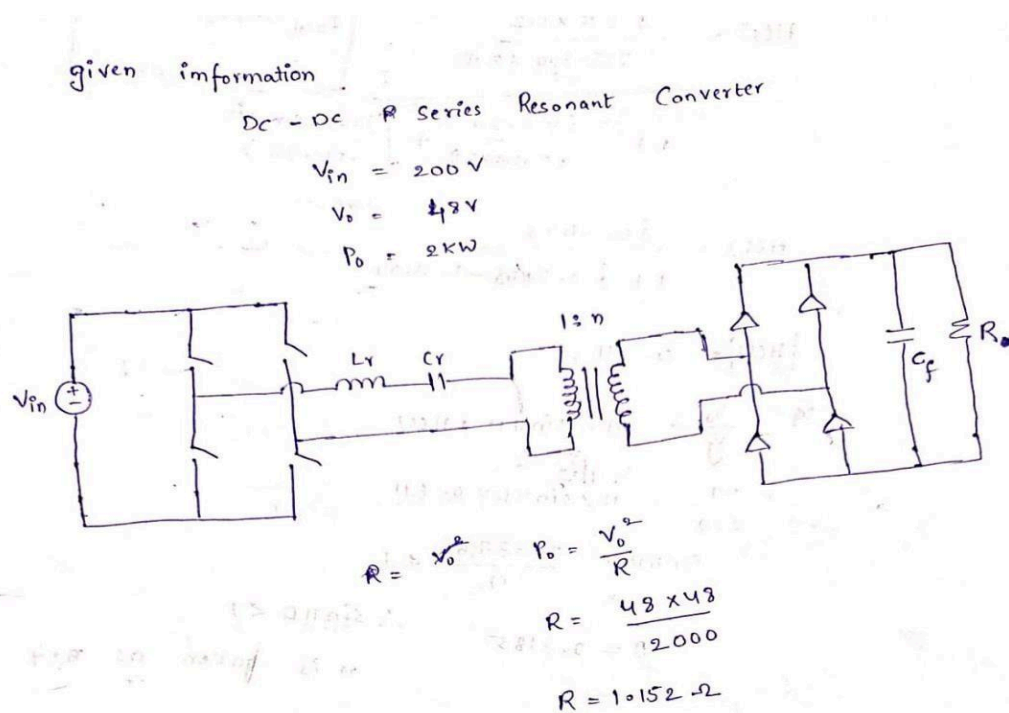

DC voltage gain

$$\frac{V_o}{V_{in}} = n \cdot H(s) \cdot \sin(\pi D)$$

$$H(s) = \frac{\frac{s}{Q_e \omega_0}}{1 + \frac{s}{Q_e \omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

take

$$Q_e = 25$$

$$f_0 = 100 \times 10^3 \text{ Hz}$$

$$\omega_0 = 2\pi f_0$$

$$= 2\pi \times 100 \times 10^3$$

$$= 6.28 \times 10^5 \text{ rad/sec}$$

$$F = f_s / f_0 = \frac{102}{100} = 1.02$$

$$H(s) = \frac{j 2\pi \times 102}{25 \times 100 \times 2\pi}$$

$$\boxed{\begin{array}{l} f_{sw} > f_0 \\ f_{sw} = 102 \text{ kHz} \end{array}}$$

$$1 + \frac{j 102 \times 2\pi}{25 \times 100 \times 2\pi} + \left(\frac{j 102 \times 2\pi}{100 \times 2\pi} \right)^2$$

$$H(s) = \frac{j 0.0408}{1 + j 0.0408 - 1.0404}$$

$$|H(s)| = 0.711$$

$$\frac{V_o}{V_g} = n \times \sin(\pi D) \times H(s)$$

$$\frac{48}{200} = n \times \sin(\pi D) \times 0.711$$

$$\sin(\pi D) = \frac{0.3376}{n} < 1$$

$$\therefore \sin(\pi D) < 1$$

$$D = 0.3135$$

n is taken as 0.4

$$n = 0.4$$

$$V_o = 0.4 \times 0.711 \times 200 \times \sin \pi D$$

$$(V_o)_{\max} = 56.88 \text{ V}$$

$$Q_e = \frac{\omega_o L}{R_e}$$

$$R_e = \frac{8}{\pi^2} R/n^2$$

$$= \frac{8}{\pi^2} \times \frac{1.152}{0.4^2}$$

$$= 5.847 \Omega$$

$$L_r = \frac{Q_e R_e}{\omega_o}$$

$$= \frac{25 \times 5.844}{2\pi \times 10^5}$$

$$= 232.6 \mu\text{H}$$

$$L_r \approx 230 \mu\text{H}$$

$$\omega_o = \frac{1}{\sqrt{L_r C_r}}$$

$$C_r = \frac{1}{L_r \omega_o^2} \Rightarrow \frac{10^6}{232.6 \times (2\pi \times 10^5)^2}$$

$$= 10.9 \text{ nF}$$

$$\approx 11 \text{ nF}$$


$$s = \frac{1}{R C_f}$$

$$C_f = \frac{1}{R \omega_{sw}/100}$$

$$= \frac{100}{1.152 \times 2\pi \times 10^2 \times 10^5}$$


$$= 135.5 \times 10^{-6} \text{ F}$$

$$C_f \approx 150 \mu\text{F}$$

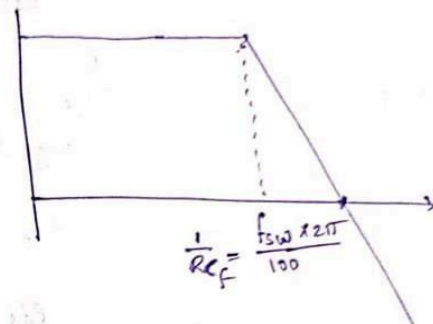

$$\begin{aligned}
 T(s) &= 4V_g \cos \pi D \left(\frac{1}{sL_r + \frac{1}{sC_r} + R_e} \right) \times \frac{2n}{\pi (sC_f + \frac{1}{R_o})} \\
 &= 4 \times 200 \times \cos(\pi \times 0.3185) \left[\frac{s \times 11 \times 10^{-9}}{s^2 (11 \times 10^{-9} \times 230 \times 10^{-6}) + 5.844 \times 11 \times 10^{-9}} + \frac{1}{s - 640.56 \times 10^3} \right] \\
 &\quad \times \frac{2 \times 0.4}{\pi \times (5150 \times 10^{-6} + \frac{1}{1.152})} \\
 &= \frac{110.11 \times 867.82 \times 10^{-4} \angle 60^\circ}{5150 \times 10^{-6} + 0.868} \\
 \boxed{T(s) = \frac{9.56 \angle 60^\circ}{5150 \times 10^{-6} + 0.868}}
 \end{aligned}$$

Bode - plot of unCompensated system

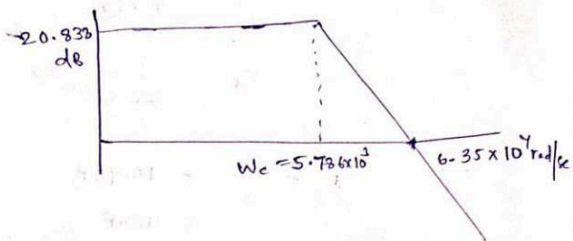

take

$$t_{ss} \leq 5 \text{ ms}$$

$$e_{ss} \leq 1\%$$

$$\frac{4}{W_{gc}} \leq 5 \times 10^{-3}$$

$$W_{gc} \geq 800 \text{ rad/sec}$$

$$e_{ss} = \lim_{s \rightarrow 0} \frac{1}{1+GH}$$

$$e_{ss} = \lim_{s \rightarrow 0} \frac{1}{1+H}$$

$$\frac{1}{1+11.01H} = 0.01$$

$$\text{dc gain of Compensator} > 9$$

$$H > 9$$

$$\text{DC Gain of } G = 11.01$$

$$W_{gc} \leq \frac{2\pi f_{sw}}{10}$$

be take
for Add PI Controller, ~~we~~ Add one Zero at $\frac{\omega_c}{10}$

And integrator,

$$K \left(\frac{s+570}{s} \right)$$


take $\omega_c = 10 \times 10^3 \text{ rad/sec}$

$$\left[\frac{K(s+570)}{s} \times \frac{9.56}{s+50 \times 10^{-6} + 0.868} \right]_{\omega_c = 10^4} = 1$$

We get $K = 0.2$


$$H(s) = \frac{s+570}{5s}$$

Bode - plot of Compensated System

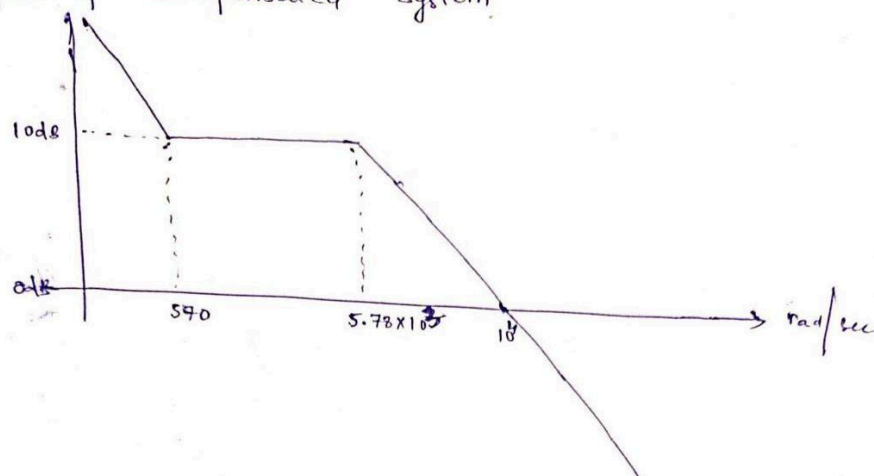


$$\begin{aligned} \text{phase margin} &= 180 + \angle G \\ &= 180 + (-6) \\ &= 174^\circ \end{aligned}$$

Simulink Model

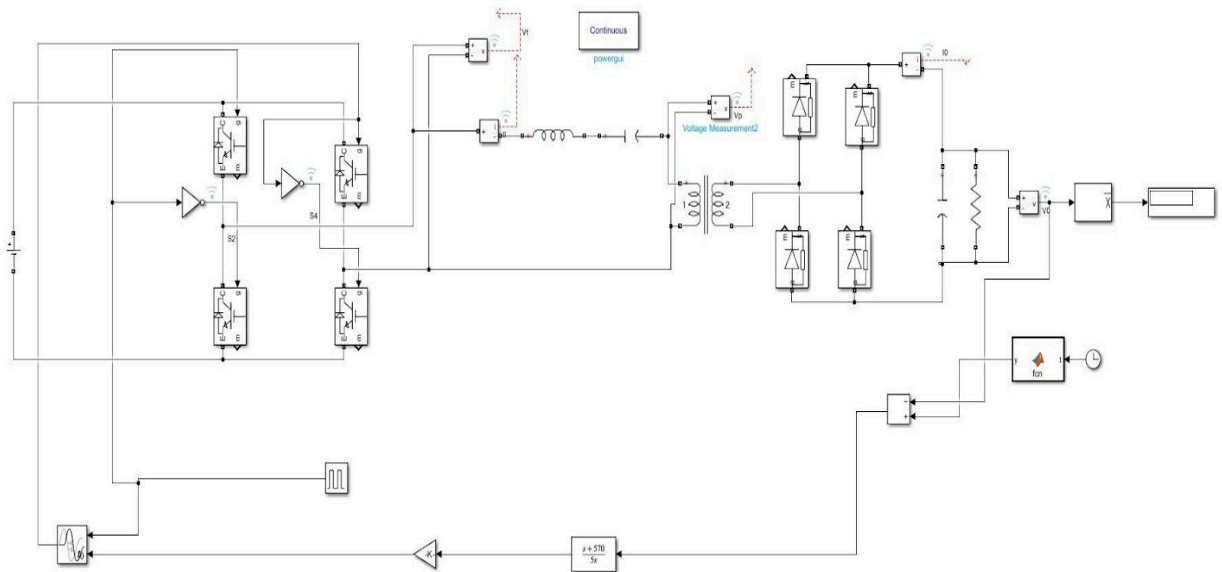


Bode Plots

Uncompensated System

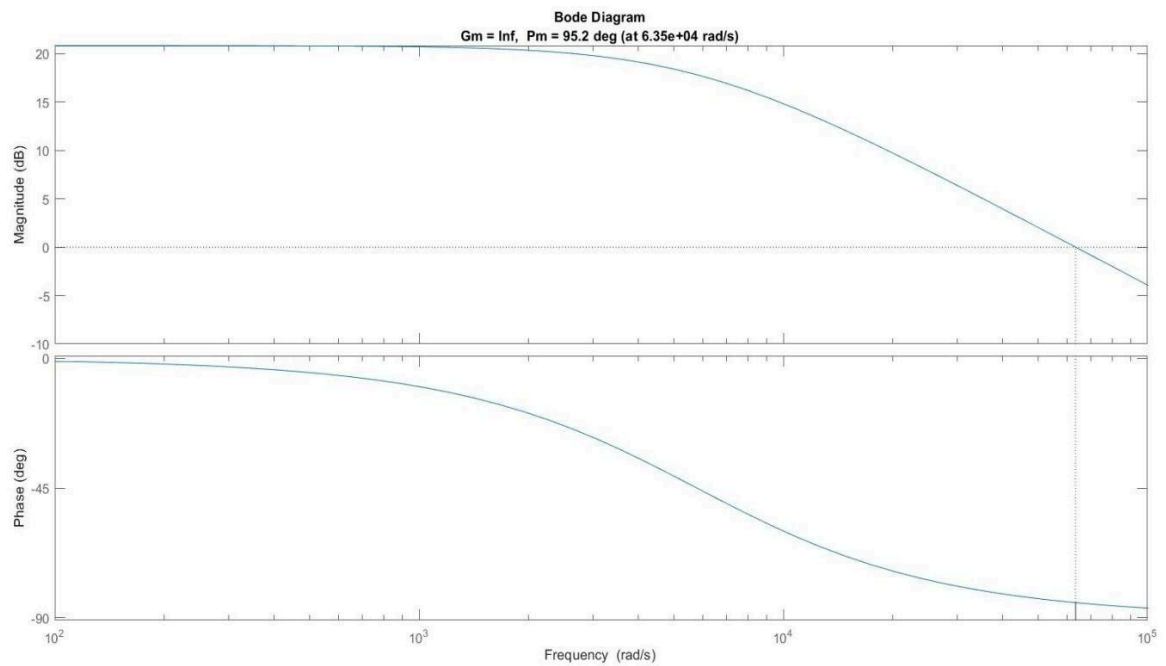


Compensated System

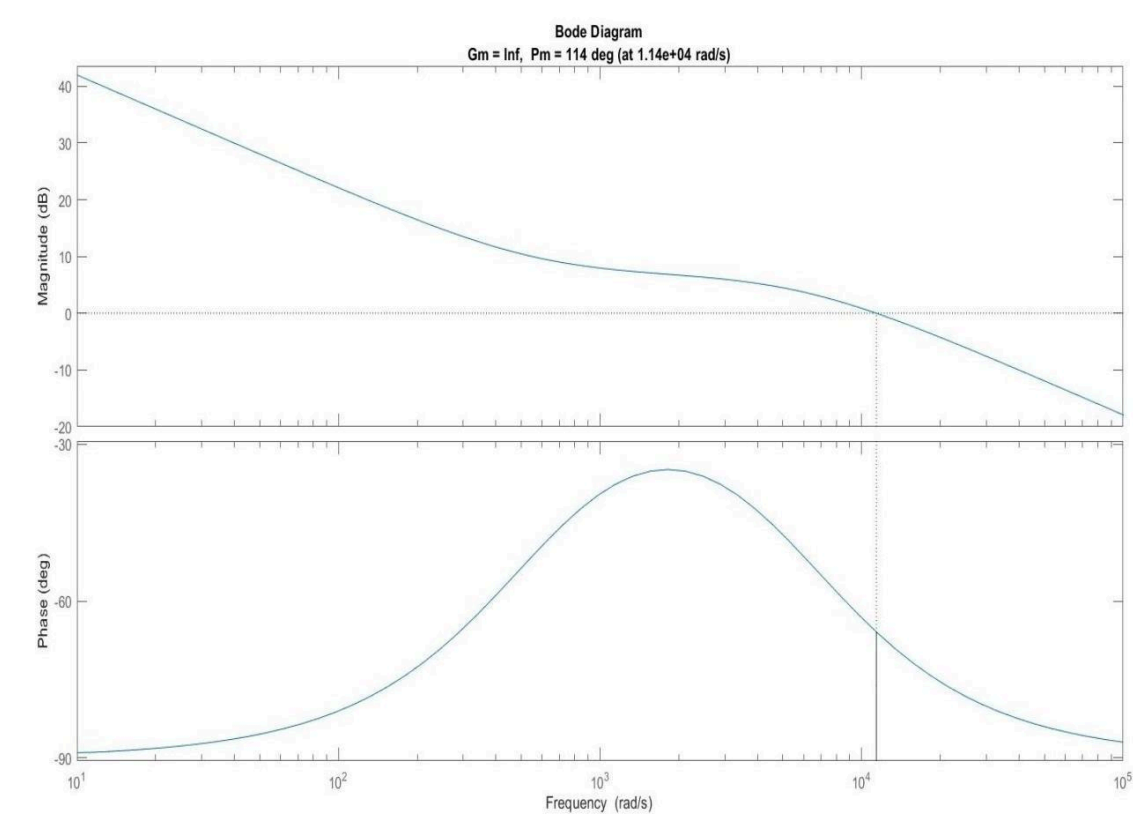


Waveforms


Output Voltage

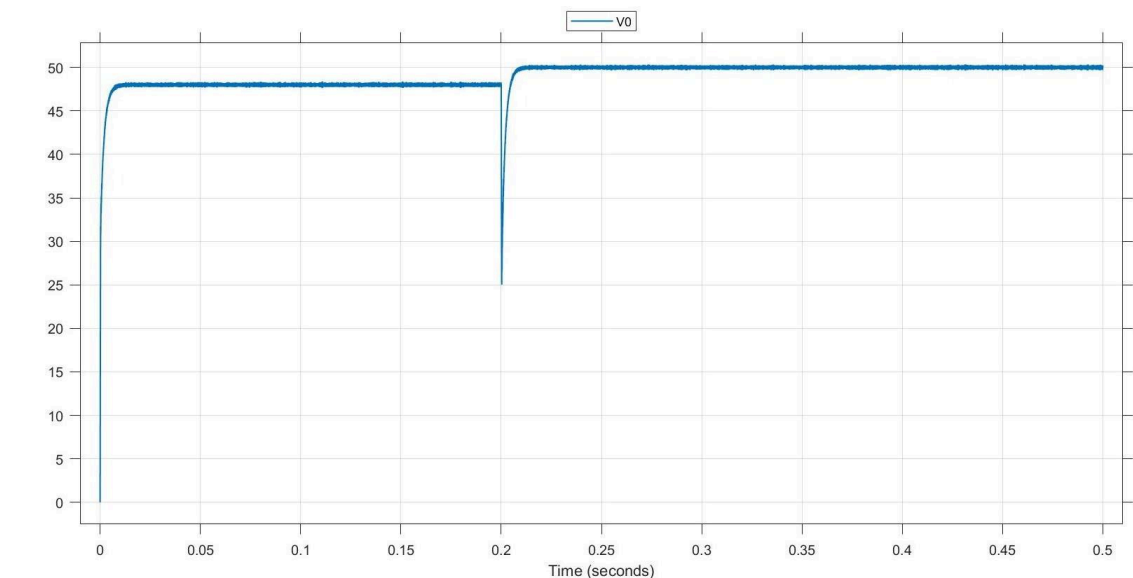


Inductor Current

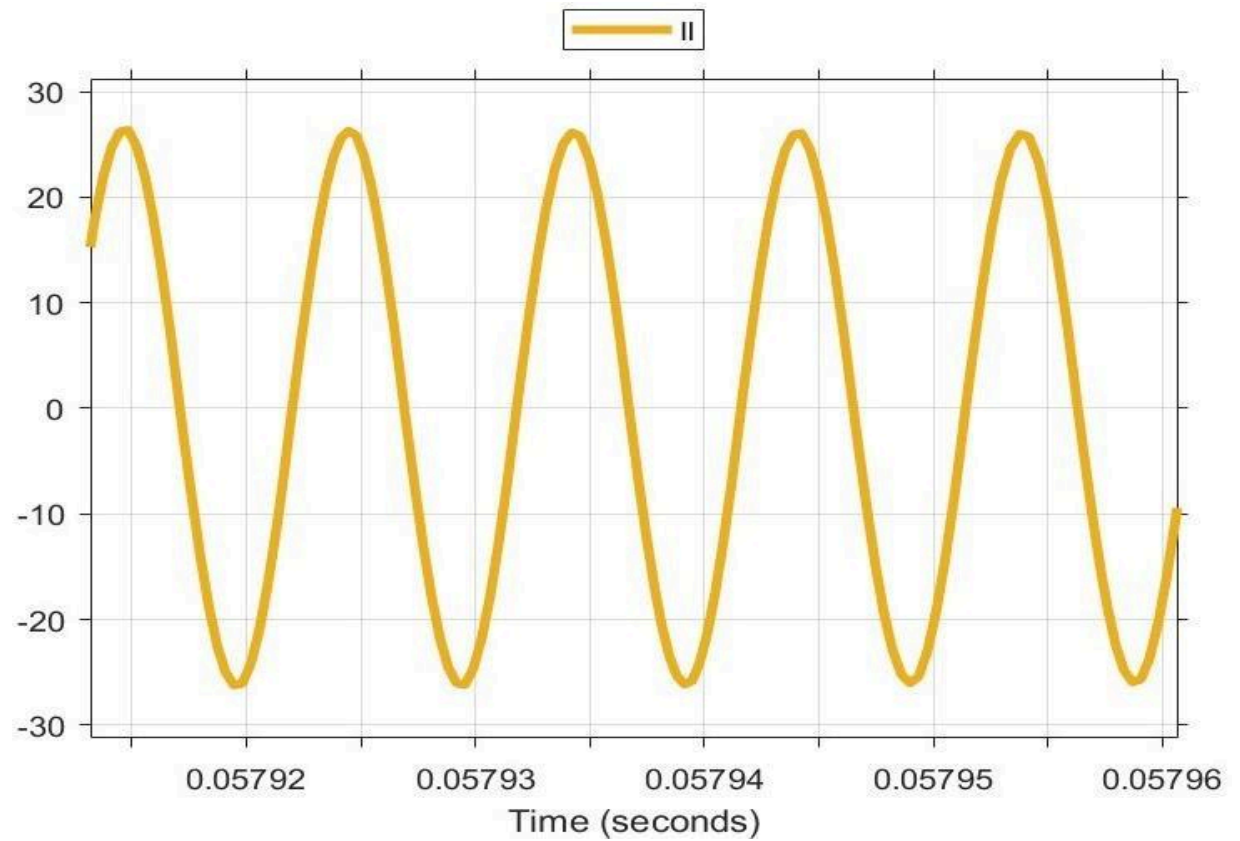


Output Current

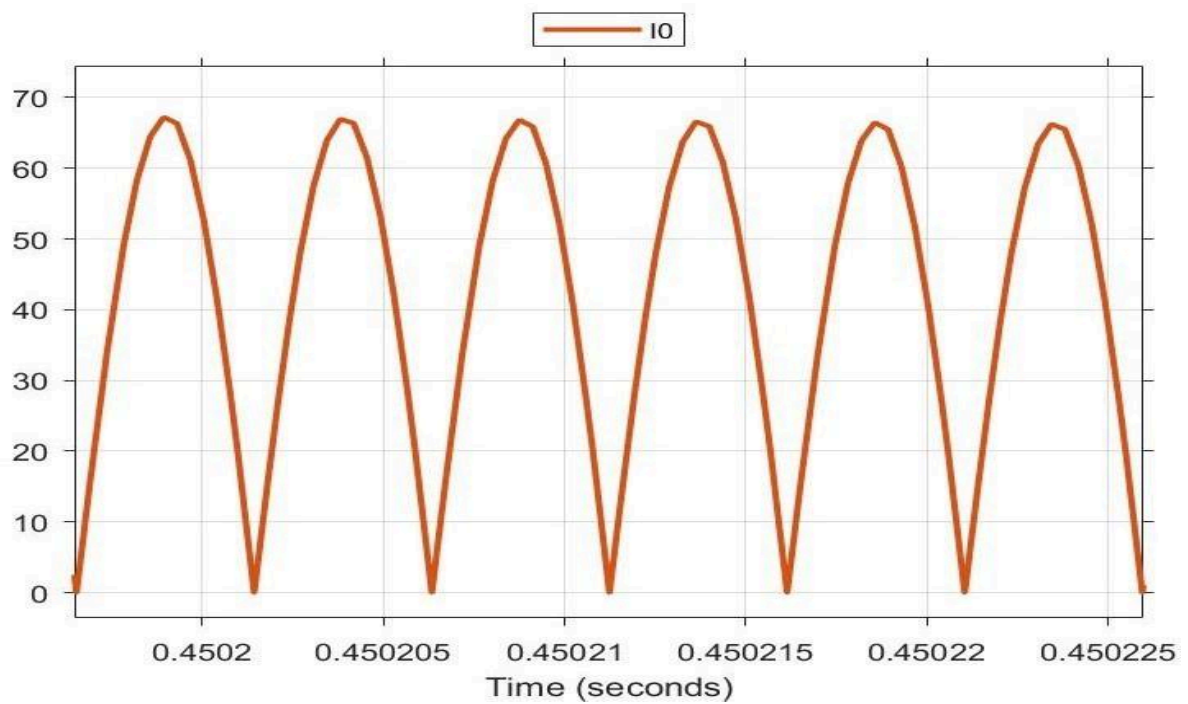

Zero Voltage Switching

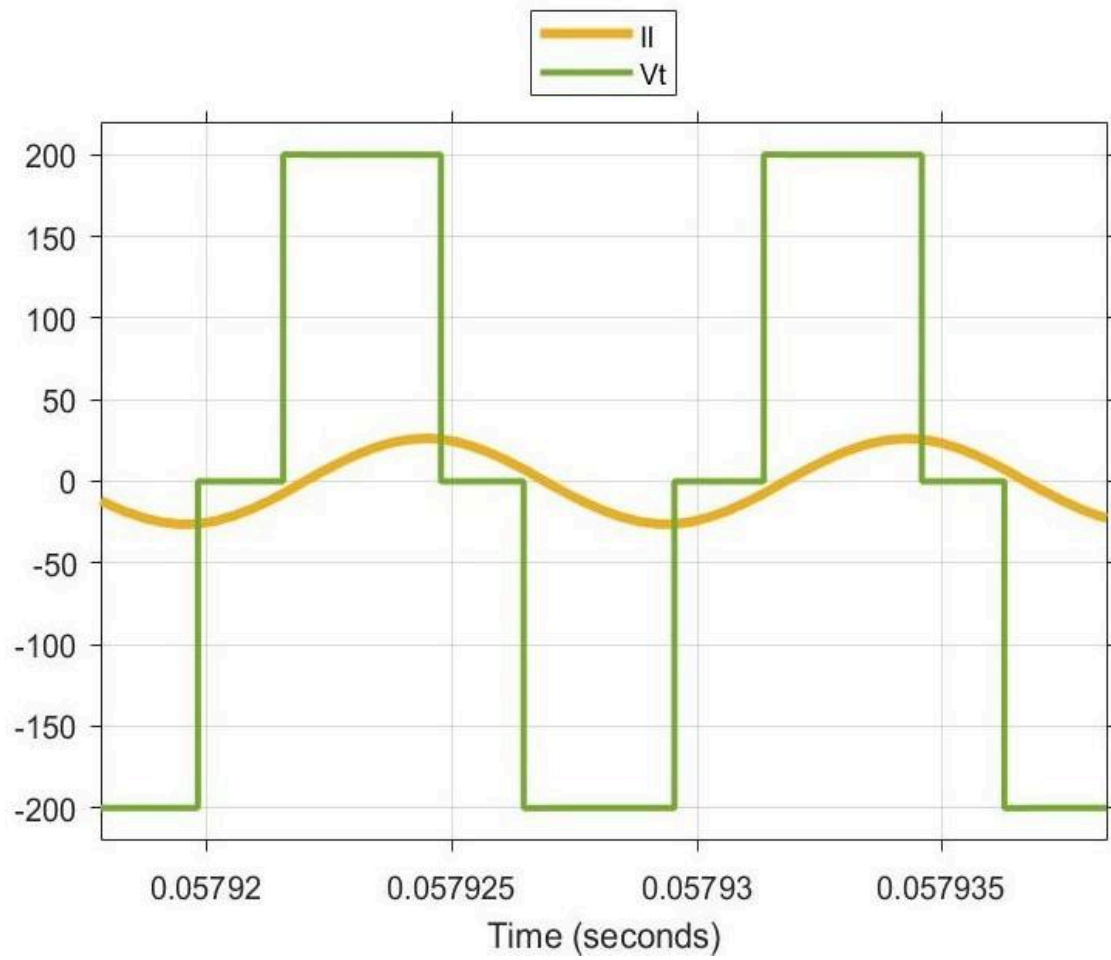

Settling Time

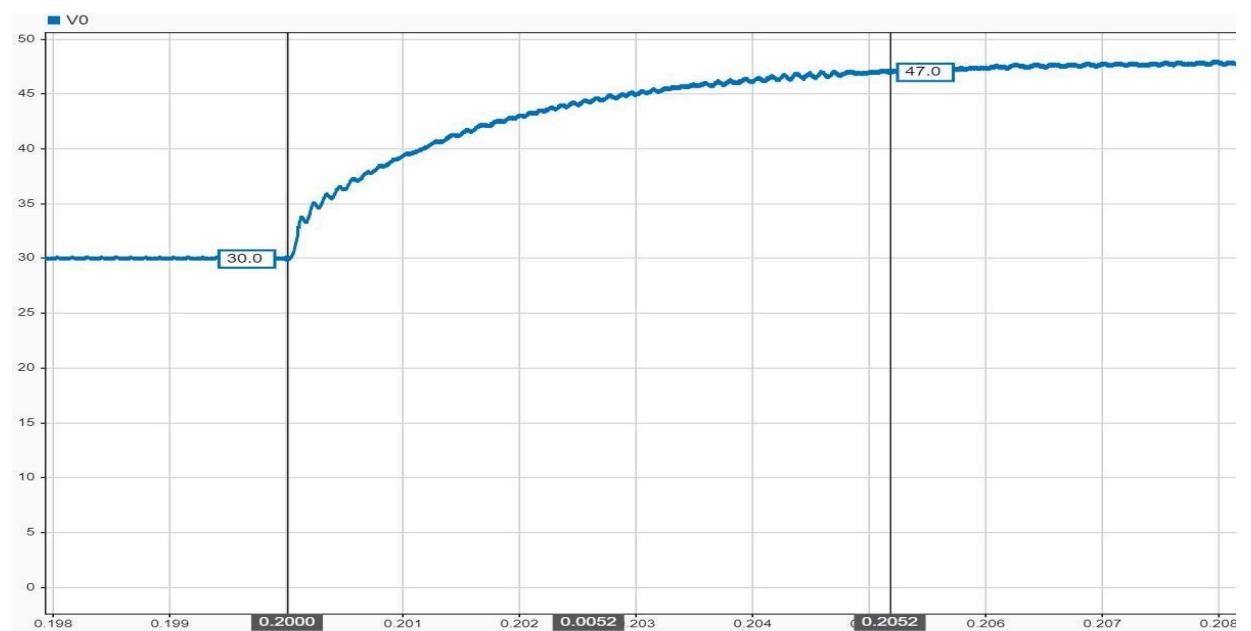

Selection of Switches

MOSFET

$$V_{DS(MAX)} = 200V$$

$$\text{Safety Factor} = 1.5$$

$$V_{DS} \text{ of switch} \geq 200 \times (1.5)$$

$$\geq 300V$$

$$\text{RMS Current of MOSFET} = 26,5/2 = 13.25A$$

$$\text{Safety Factor} = 2$$

$$I_{RMS} \text{ rating} \geq 13.25 \times 2$$

$$\geq 26.5A$$

Data Sheet :

https://www.mouser.in/datasheet/2/308/1/FDB28N30TM_D-2311897.pdf

Diode

$$PIV = 48V$$

$$\text{Safety Factor} = 1.5$$

$$\text{Voltage rating of Diode} \geq 72V$$

$$\text{Average current of Diode} = 20.38A$$

$$\text{Safety Factor} = 1.5$$

$$I_{RMS} \text{ rating} \geq 20.38 \times 1.5$$

$$\geq 30.57A$$

Data Sheet :

<https://www.vishay.com/doc?89169>